



**MODEL ANSWER**

**SUMMER – 2018 EXAMINATION**

**Subject: Basic Electronics**

**Subject Code: 22225**

**Important Instructions to examiners:**

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No	Sub Q.N.	Answer	Marking Scheme
1.	(a) Ans.	<b>Attempt any FIVE of the following:</b> <b>List any four specifications of resistors.</b> <b>Specifications of resistors:</b> <ul style="list-style-type: none"><li>• Resistance Value / Resistivity</li><li>• Tolerance</li><li>• Power Rating</li><li>• Thermal Stability</li><li>• Maximum operating temperature</li><li>• Maximum operating voltage</li></ul>	<b>10</b> <b>2M</b>  <i>Any four specifications</i> <i>½M each</i>
	(b) Ans.	<b>State the need of filters in a regulated DC power supply.</b> <b>Need of filters:</b> The output of a rectifier contains dc component as well as ac component. The presence of the ac component is undesirable and must be removed so that pure dc can be obtained. Filter circuits are used to remove or minimize this unwanted ac component of the rectifier output and allows only the dc component to reach the load.	<b>2M</b>  <i>Relevant need</i> <b>2M</b>





MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225
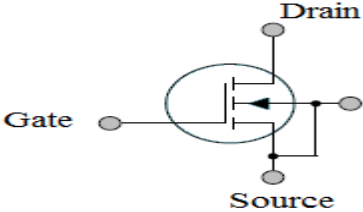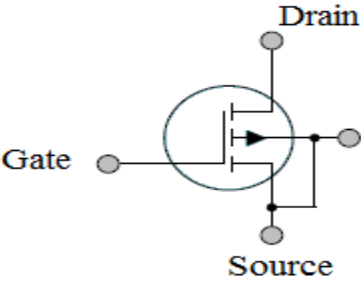
<p>(c) Ans.</p>	<p><b>Define <math>\alpha</math> and <math>\beta</math> of transistor.</b> <b><math>\alpha</math> (Alpha)</b> : This is the Common Base dc current gain. It defined as the ratio of collector current (<math>I_C</math>) to emitter current (<math>I_E</math>). <math display="block">\alpha = \frac{I_C}{I_E}</math><b><math>\beta</math> (Beta)</b>: This is the Common Emitter dc current gain. It is defined as the ratio of collector current (<math>I_C</math>) to the base current (<math>I_B</math>). <math display="block">\beta = \frac{I_C}{I_B}</math></p>	<p>2M  <i>Each definition 1M</i></p>
<p>(d) Ans.</p>	<p><b>Draw the symbol of N-channel and P-channel enhancement type MOSFET.</b> <b>Symbol of N- Channel Enhancement MOSFET:</b>  <b>Symbol of P- Channel Enhancement MOSFET:</b> </p>	<p>2M  <i>Each symbol 1M</i></p>
<p>(e) Ans.</p>	<p><b>List the types of signals.</b> <b>Types of signals:</b> 1. Analog signal 2. Digital signal 3. AC signal 4. DC signal 5. Sinusoidal signal 6. Triangular signal 7. Square signal</p>	<p>2M  <i>Any 2 types 1M each</i></p>









**MODEL ANSWER**

**SUMMER – 2018 EXAMINATION**

**Subject: Basic Electronics**

**Subject Code: 22225**

		<b>Output Impedance</b>	High <b>OR</b> 50 K $\Omega$	Medium <b>OR</b> 10K $\Omega$ to 50K $\Omega$	Low <b>OR</b> 50 $\Omega$	<i>Correct comparison 1M each</i>
		<b>Current Gain</b>	Less than or equal to 1 <b>OR</b> $\alpha = \frac{I_C}{I_E}$	High (100) <b>OR</b> $\beta = \frac{I_C}{I_B}$	High (100) <b>OR</b> $\gamma = \frac{I_E}{I_B}$	
		<b>Application</b>	High frequency Circuits	Audio frequency circuits (Amplifiers)	Impedance Matching	
<b>3.</b>	<b>(a)</b> <b>Ans.</b>	<p><b>Attempt any THREE of the following:</b> <b>Draw and explain the construction of N-channel JFET.</b></p> <div style="text-align: center;"> <p>The diagram shows a cross-section of an N-channel JFET. It consists of a central n-type silicon bar (Channel) flanked by two p-type regions (Gate). The top of the bar is labeled 'Drain' and the bottom is labeled 'Source'. The two p-type regions are connected to a common terminal labeled 'Gate'. The p-type regions are also labeled 'p-type'.</p> </div> <p><b>Construction Details:</b> A JFET consists of a p-type or n-type silicon bar containing two PN junctions at the sides as shown in fig. The bar forms the conducting channel for the charge carriers. If the bar is of p-type, it is called p-channel JFET and if the bar is of n-type, it is called n-channel JFET as shown in fig. The two PN junctions forming diodes are connected internally and a common terminal called gate is taken out. Other terminals are source and drain taken out from the bar as shown in fig.1. Thus a JFET has three terminals such as, gate (G), source (S) and drain (D).</p>				<p><b>12</b> <b>4M</b></p> <p style="text-align: center;"><i>Diagram 2M</i></p> <p style="text-align: center;"><i>Explanation 2M</i></p>



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION  
(Autonomous)  
(ISO/IEC - 27001 - 2005 Certified)

MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225

	<p>(b) Ans.</p>	<p><b>State any four selection criteria for transducers.</b> <b>Selection criteria for transducers are:</b> 1. Operating range 2. Operating principle 3. Sensitivity 4. Accuracy 5. Frequency response and resonant frequency 6. Errors 7. Environmental compatibility 8. Usage and ruggedness. 9. Electrical aspect. 10. Stability and Reliability 11. Loading effect 12. Static characteristics 13. General selection criteria</p>	<p>4M  <i>Any four points 1M each</i></p>
	<p>(c) Ans.</p>	<p><b>Determine the value of resistance with the following colour code:</b> <b>(i) Red, Red, Orange, Gold (ii) Brown, Black, Black, Silver</b> <b>(i) Red, Red, Orange, Gold</b></p> <p style="text-align: center;">Red      Red      Orange      Gold ↓        ↓        ↓        ↓ 2        2        x 1000    ± 5%</p> <p style="text-align: center;">= 22 x 1000 ± 5%</p> <p>Value of resistor is <span style="border: 1px solid black; padding: 2px;">22 KΩ + 5%</span> OR <span style="border: 1px solid black; padding: 2px;">22000Ω + 5%</span></p> <p><b>(ii) Brown, Black, Black, Silver</b></p> <p style="text-align: center;">Brown    Black    Black    Silver ↓        ↓        ↓        ↓ 1        0        x 1        ±10%</p> <p style="text-align: center;">= 10 x 1 ± 10%</p> <p>Value of resistor is <span style="border: 1px solid black; padding: 2px;">10 Ω ± 10%</span></p>	<p>4M  <i>Each bit 2M</i></p>




MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225

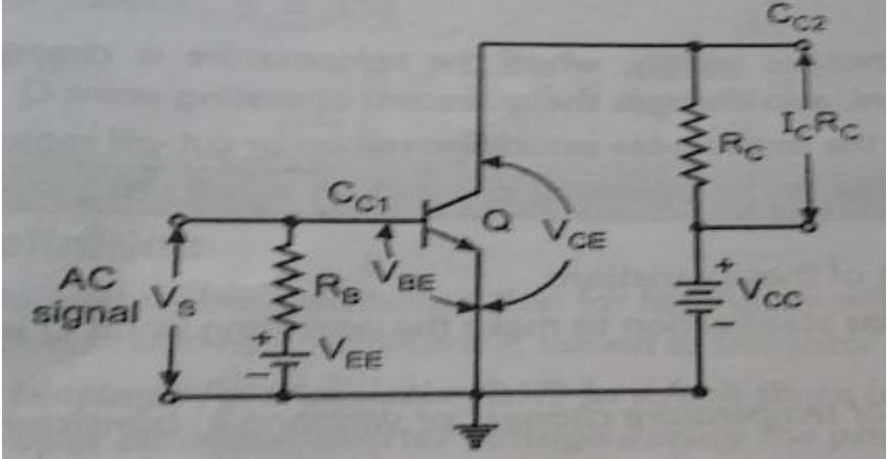	<p>(d)</p> <p>Ans.</p>	<p><b>Explain the concept of DC load line and operating point for biasing circuit.</b></p> <p><b>DC load line:</b> The straight line drawn on the characteristics of a BJT amplifier which give the DC values of collector current <math>I_C</math> and collector to emitter voltage <math>V_{CE}</math> corresponding to zero signal i.e. DC conditions is called DC load line.</p>  <p>To plot <math>I_{C(MAX)}</math>, <math>V_{CE (MAX)}</math> on output characteristics:</p> <p>Get <math>V_{CE (MAX)}</math> by putting <math>I_c = 0</math></p> $V_{CE} = V_{CC} - I_c R_c$ $V_{CE (MAX)} = V_{CC} \quad \text{since } I_c = 0$ <p>Get <math>I_{C(MAX)}</math> by putting <math>V_{CE} = 0</math></p> $I_{C(MAX)} = \frac{V_{CC}}{R_c}$	<p>4M</p> <p>1M</p> <p>1M</p>
--	------------------------	--	-------------------------------



**MODEL ANSWER**

**SUMMER – 2018 EXAMINATION**

**Subject: Basic Electronics**

**Subject Code: 22225**

		<b>1M</b>
	<p><b>Operating point or Q- point:</b> The fixed levels of certain currents and voltages in a transistor in active region defines the operating point on the DC load line.</p> <p>For normal operation of the transistor, the Q- point is to be selected at the center of the load line.</p>	<b>1M</b>
<b>4.</b>	<p><b>(a)</b> <b>Ans.</b></p> <p><b>Attempt any THREE of the following:</b> <b>Explain:</b> <b>(i) Seebeck effect      (ii) Peltier effect</b></p> <p><b>(i) Seebeck effect:</b> Seebeck effect states that whenever two dissimilar metals are connected together to form two junctions out of which, one junction is subjected to high temperature and another is subjected to low temperature then e.m.f is induced proportional to the temperature difference between two junctions.</p> <div style="text-align: center;"> </div> <p style="text-align: center;"><b>Fig. Seedback effect</b></p>	<b>12</b> <b>4M</b>  <b>Seeback effect</b> <b>2M</b>

**MODEL ANSWER**

**SUMMER – 2018 EXAMINATION**

**Subject: Basic Electronics**

**Subject Code: 22225**

	<p><b>(ii) Peltier effect:</b> Peltier effect state that for two dissimilar metals closed loop, if current forced to flow through the closed loop then one junction will be heated and other will become cool.</p> <div style="text-align: center;"> </div>	<p><i>Peltier effect</i> <b>2M</b></p>
<p><b>(b)</b>  <b>Ans.</b></p>	<p><b>Draw the basic block diagram of regulated DC power supply. Explain the function of each block.</b></p> <div style="text-align: center;"> </div> <p style="text-align: center;"><b>Block diagram of regulated power supply</b></p> <p>1. TRANSFORMER: Transformer works on the basis of ELECTROMAGNETIC INDUCTION and they are mainly classified into two:</p> <ol style="list-style-type: none"> <li>i. STEP UP TRANSFORMER</li> <li>ii. STEPDOWN TRANSFORMER</li> </ol> <p>Step up transformer up convert the input voltage where step down transformer down converts. For a DC Power Source we have to use</p>	<p><b>4M</b></p> <p style="text-align: right;"><i>Diagram</i> <b>2M</b></p> <p style="text-align: right;"><i>Explanation</i> <b>2M</b></p>



MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225

	<p>step down transformers, to convert the high voltage AC supply to low voltage DC.</p> <p>2. RECTIFIER: Rectifiers are used to convert the sinusoidal AC voltage to non-sinusoidal pulsating DC. The main component used in Rectifiers are diodes due to its switching action. They will conduct Current only in one direction, hence the voltage. So we can use them as rectifiers to make the alternating Current unidirectional. Rectifiers are classified into Three :-</p> <ul style="list-style-type: none"><li>i. HALF WAVE RECTIFIERS</li><li>ii. FULL WAVE RECTIFIERS</li><li>iii. BRIDGE RECTIFIERS</li></ul> <p>3. FILTERS: Filters are used to eliminate or filter-out the unwanted ripples from the rectified output. Filters play an important role in dc Power supplies, they make the pulsating dc steady.</p> <p>4. VOLTAGE REGULATOR: Voltage Regulators are used to regulate the output Voltage over load. They make the Voltage unvaried with load connected to it. This will eliminates the remaining ripples from the filter output. The output from Voltage Regulator may be the required DC. Voltage Regulators includes some safety measures such as Current Limiting, short circuit etc.</p>	
<p>(c) Ans.</p>	<p><b>Describe the working of transistor as a switch with circuit diagram.</b></p> <div data-bbox="438 1407 1201 1827" data-label="Diagram"></div>	<p>4M</p>

Transistor as a Switch Circuit Diagram



MODEL ANSWER

SUMMER – 2018 EXAMINATION


Subject: Basic Electronics

Subject Code: 22225

From the above circuit we can see that the control input  $V_{in}$  is given to base through a current limiting resistor  $R_b$  and  $R_c$  is the collector resistor which limits the current through the transistor. In most cases output is taken from collector but in some cases load is connected in the place of  $R_c$ .

- ON = Saturation
- OFF = Cutoff

Transistor as a Switch – ON:

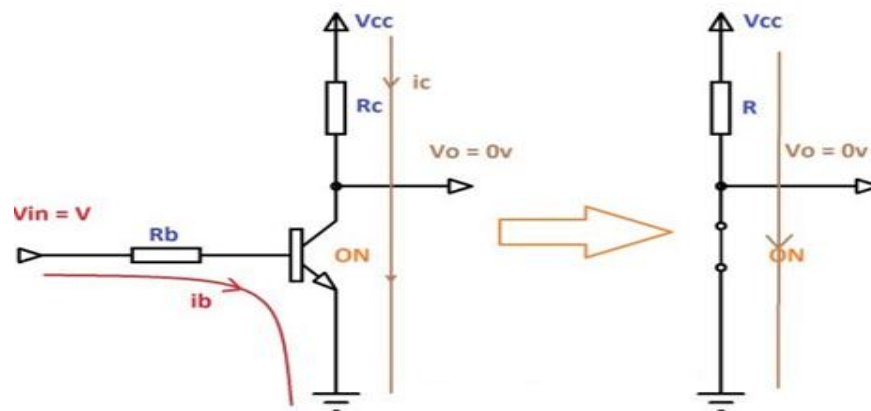

Transistor as a Switch ON

Transistor will become ON (saturation) when a sufficient voltage  $V$  is given to input. During this condition the Collector Emitter voltage  $V_{ce}$  will be approximately equal to zero, i.e. the transistor acts as a short circuit. For a silicon transistor it is equal to 0.3v. Thus collector current  $I_c = V_{cc}/R_c$  will flow.

ON  
switch  
2M








**MODEL ANSWER**

**SUMMER – 2018 EXAMINATION**

**Subject: Basic Electronics**

**Subject Code: 22225**

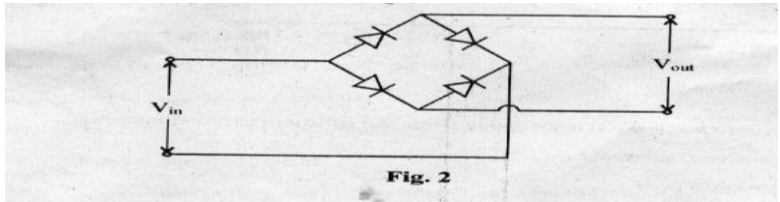		<p><b>For sine waveform:</b></p> <ol style="list-style-type: none"> <li>1. Peak to peak amplitude = 10 V</li> <li>2. Frequency = <math>1/T = 1/(2.5\text{ms}) = 400 \text{ Hz}</math></li> <li>3. wavelength <math>\lambda = Vc/f = (3*10^8)/400 = 750000 \text{ m}</math></li> </ol> <p><b>For square waveform:</b></p> <ol style="list-style-type: none"> <li>1. Peak to peak amplitude = 20 V</li> <li>2. Frequency = <math>1/T = 1/(20 \text{ ms}) = 50 \text{ Hz}</math></li> <li>3. wavelength <math>\lambda = Vc/f = (3*10^8)/50 = 6000000 \text{ m}</math></li> </ol>	<p><i>Each calculation 1M</i></p>
	<p>(b) <b>Ans.</b></p>	<p><b>In CE configuration, if <math>\beta = 100</math>, leakage current <math>I_{CEO} = 150 \mu\text{A}</math>. If the base current is 0.2 mA, calculate the value of <math>I_C</math>, <math>I_E</math> and <math>\alpha</math>.</b> (Note: Marks should be given for correct formula)</p> <p>Given data: <math>\beta = 100</math>, <math>I_{CEO} = 150 \mu\text{A}</math>, <math>I_B</math> is 0.2mA , To find <math>I_C</math>, <math>I_E</math> and <math>\alpha</math>.</p> <p><b>Solution :-</b> We know</p> <ol style="list-style-type: none"> <li>1) <math>\alpha = \beta / (\beta + 1)</math> <math>= 100/(100+1) = 0.99</math></li> <li>2) <math>I_C</math> is given as, <math display="block">I_C = \beta * I_B + I_{CEO}</math><math display="block">= (100 * 0.2 * 10^{-3}) + 150 * 10^{-6} = 20.150 \text{ mA.}</math></li> <li>3) <math>I_E</math> is given as, <math display="block">I_E = I_C + I_B = (20.150 + 0.2) \text{ mA} = 20.35 \text{ mA}</math></li> </ol>	<p>6M</p> <p><i>2M for correct calculation of each parameter (Formula 1M, Calculation -1M)</i></p>
	<p>(c) <b>Ans.</b></p>	<p><b>Identify the circuit shown in Fig. 2 and explain working with input-output waveforms for a sinusoidal input.</b></p> <div style="text-align: center;">  <p>Fig. 2</p> </div> <p>The given circuit is Bridge rectifier– (with diodes numbered)</p>	<p>6M</p>








MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225

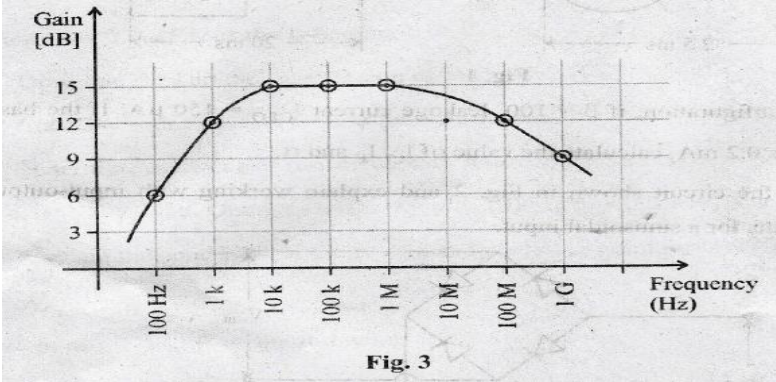	<p>Ans.</p>	<p><b>Determine:</b> <b>(i) AC drain resistance</b> <b>(ii) Transconductance</b> <b>(iii) Amplification factor</b> <i>(Note: Formula should be given marks)</i></p> <p><b>(i) AC drain resistance</b> is given as, <math>r_d = \frac{\Delta V_{DS}}{\Delta I_D}</math> at <math>V_{GS}</math> constant</p> $\frac{15V-7V}{10.25-10mA} = \frac{8V}{0.25mA} = 32K\Omega$ <p><b>(ii) Transconductance</b> <math>g_m</math> is given as, <math>g_m = \frac{\Delta I_D}{\Delta V_{GS}}</math>, <math>V_{DS}</math> at constant</p> $\frac{10.25mA-9.65mA}{0-(-0.2V)} = \frac{0.6mA}{0.2V} = 3m\text{ Mho}$ <p><b>(iii) Amplification factor</b> <math>\mu</math></p> $\mu = r_d \times g_m = 32\text{ K}\Omega \times 3m\text{ Mho} = 96$	<p>2M for each (1M for Formula, 1M for calculation)</p>
	<p>Ans.</p>	<p><b>(b)</b> Observe the given frequency response of RC coupled amplifier in Fig. 3 Calculate: <b>(i) Lower cut-off frequency (<math>F_L</math>)</b> <b>(ii) Higher cut-off frequency (<math>F_H</math>)</b> <b>(iii) Bandwidth (BW)</b></p>  <p>Fig. 3</p>	<p>6M</p>



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION  
(Autonomous)  
(ISO/IEC - 27001 - 2005 Certified)

MODEL ANSWER

SUMMER – 2018 EXAMINATION

Subject: Basic Electronics

Subject Code: 22225

		As maximum gain is 15 dB, 3 dB down gain is 12 dB. So, (i) The lower cut-off frequency $F_L = 1\text{KHz}$  (ii) Higher cut-off frequency $F_H = 100\text{ MHz}$  (iii) Bandwidth (BW) = $F_H - F_L = (100000 - 1)\text{KHz} = 99999\text{ KHz}$	<i>2M for each proper answer</i>
	(c)  <b>Ans.</b>	<b>Identify active and passive transducer from the following transducers:</b> (i) <b>Capacitive transducer</b> (ii) <b>Photovoltaic cells</b> (iii) <b>Piezoelectric transducer</b> (iv) <b>Strain gauge</b> (v) <b>Thermocouple</b> (vi) <b>Thermistors</b> (i) Capacitive transducer-passive transducer (ii) Photovoltaic cells- active transducer (iii) Piezoelectric transducer–active transducer. (iv) Strain gauge-passive transducer (v) Thermocouple- active transducer (vi) Thermistors- passive transducer	6M  <i>1M each for right answer</i>